
# Amateur Radio Satellite Transceiver (SKY130)

Thomas Parry

April 7, 2021

#### System Goal

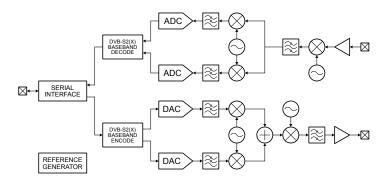

- Amateur radio satellite transceiver
- Microwave bands 2.4 GHz, 5.8 GHz and 10.2 GHz
- Payload data to antenna and back




MPW-A

MPW-B 0000000


#### MPW-A

# System View

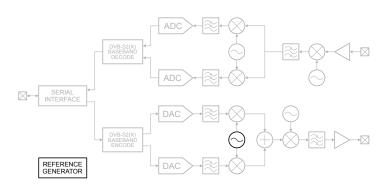

Bandgap Reference

# Bandgap Topology

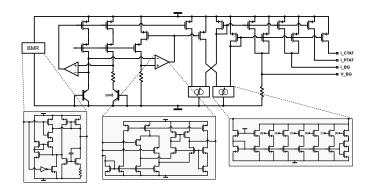


- Separate PTAT and CTAT with 6-bits trimming
- Less than  $\pm 0.2\%$  variation from  $-40^{\circ}$  to  $125^{\circ}$



MPW-A ○ ○ ○ ○ ○ ○ ○ ○


Bandgap Reference

# Bandgap Layout

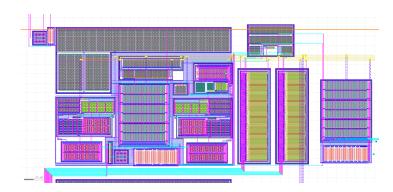

Phase Locked Loop

## PLL Topology

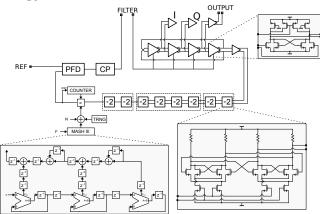

- 1.3 3.6 GHz differential quadrature output range
- CML and FF pre-scalars, third-order MASH modulator with TRNG dither
- Off chip compensation filter




MPW-A

○○
○○
○○
○○

MPW-B 000000

Phase Locked Loop

# PLL Layout

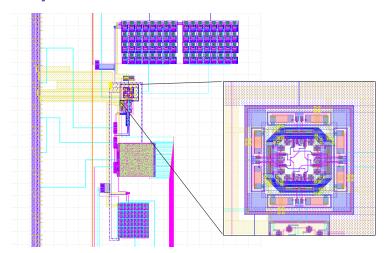


Tools

#### Tools

Tools

## Schematic Capture

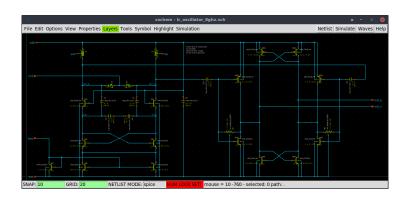


 ${\sf xschem-github.com/StefanSchippers/xschem}$ 



MPW-A ○○ ○○ ○○ ○○

Tools

### Layout

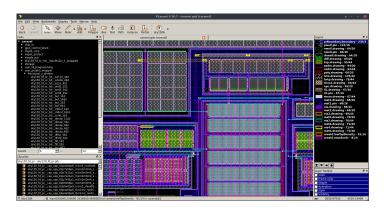

KLayout - klayout.de

Magic - opencircuitdesign.com/magic



Tools

#### Simulation

Open source Spice simulators:

- NGSpice
- Xyce

Command line interface only



Tools

## Python


#### Components plugged together using Python.

- Device characterisation and querying
- Automated simulation
- Post-processing measurement
- Unit tests (OpenHTF / pytest)




#### MPW-B

#### Aim

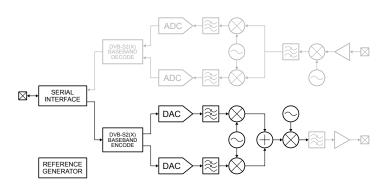


#### **DAC Topology**

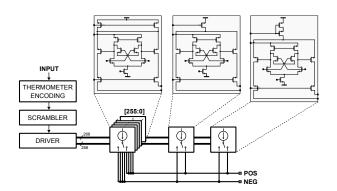

- 10-bit current steered differential DAC
- Mismatch scrambling




## Mixer Topology

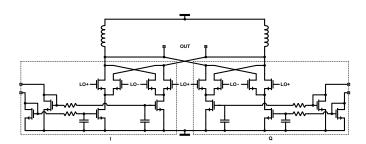

- Current inputs
- Single pole low pass filter
- Baseband to L band




# Oscillator Topology

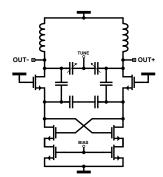

- Colpitts based topology
- 8 GHz nominal



### DVB-S2(X) Baseband Modulator

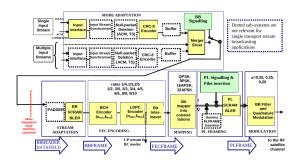


- LDPC + BCH forward error correction
- Modulation
- Near Shannon limit operation

Phase4 project: phase4space.github.io



## System Goal

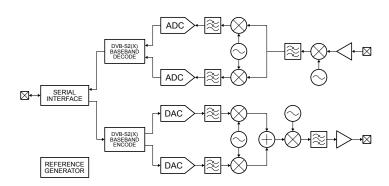

#### **Thanks**

yrrapt@gmail.com @yrrapt on Skywater Slack channel